

| Rule                    | Expression   |
|-------------------------|--|
| Commutativity           | $X + Y = Y + X$<br>$X \cdot Y = Y \cdot X$   |
| Associativity           | $(X + Y) + Z = X + (Y + Z)$<br>$(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$   |
| Distributivity          | $X \cdot Y + X \cdot Z = X \cdot (Y + Z)$<br>$(X + Y) \cdot (X + Z) = X + Y \cdot Z$   |
| Covering                | $X + X \cdot Y = X$<br>$X \cdot (X + Y) = X$   |
| Combining               | $X \cdot Y + X \cdot Y = X$<br>$(X + Y) \cdot (X + Y) = X$   |
| Consensus               | $X \cdot Y + X \cdot Z + Y \cdot Z = X \cdot Y + X' \cdot Z$<br>$(X + Y) \cdot (X + Z) \cdot (Y + Z) = (X + Y) \cdot (X + Z)$  |
| Generalized Idempotency | $X + X + \dots + X = X$<br>$X \cdot X \cdot \dots \cdot X = X$   |
| DeMorgan's Theorems     | $(X_1 \cdot X_2 \cdot \dots \cdot X_n)' = X_1' + X_2' + \dots + X_n'$<br>$(X_1 + X_2 + \dots + X_n)' = X_1' \cdot X_2' \cdot \dots \cdot X_n'$   |
| Generalized DeMorgan's  | $F(X_1, X_2, \dots, X_n, +, \cdot) = F(X_1, X_2, \dots, X_n, \cdot, +)'$   |
| Shannon's Expansion     | $F(X_1, X_2, \dots, X_n) = X_1 \cdot F(1, X_2, \dots, X_n) + X_1' \cdot F(0, X_2, \dots, X_n)$<br>$F(X_1, X_2, \dots, X_n) = [X_1 + F(0, X_2, \dots, X_n)] \cdot [X_1' + F(1, X_2, \dots, X_n)]$ |
| Dual                    | Interchange + with $\cdot$ , and 0 with 1  |

```
//      ! : Logical NOT, ~ : Bitwise NOT
//      && : Logical AND, & : Bitwise AND
//      || : Logical OR,  | : Bitwise OR
//      ^  : Bitwise XOR
//      ^^ : Bitwise XNOR
//      == : Equality,    === : Case Equality (4-state)
//      != : Inequality,  !== : Case Inequality (4-state)
```

```
module my_module (
    input  logic clk,    // clock
    input  logic rst,    // reset
    output logic out
);
    // Module internals here
endmodule
```

```
// Sequential (synchronous) logic
always_ff @(posedge clk or posedge rst) begin
    if (rst)
        out <= 0;
    else
        out <= ~out;
end

// Combinational logic
always_comb begin
    // assignments that depend solely on input combinatorics
end
```

```
interface simple_if (input logic clk);
    logic data;
    modport master (output data);
    modport slave  (input  data);
endinterface
```

```
property p_reset;
    @(posedge clk) disable iff (rst) (a |-> b);
endproperty

assert property(p_reset);
```

Buffer

| A | Output |
|---|--------|
| 0 | 0      |
| 1 | 1      |



NOT

| A | Output |
|---|--------|
| 0 | 1      |
| 1 | 0      |



OR

| A | B | Output |
|---|---|--------|
| 0 | 0 | 0      |
| 0 | 1 | 1      |
| 1 | 0 | 1      |
| 1 | 1 | 1      |



AND

| A | B | Output |
|---|---|--------|
| 0 | 0 | 0      |
| 0 | 1 | 0      |
| 1 | 0 | 0      |
| 1 | 1 | 1      |



NAND

| A | B | Output |
|---|---|--------|
| 0 | 0 | 1      |
| 0 | 1 | 1      |
| 1 | 0 | 1      |
| 1 | 1 | 0      |



NOR

| A | B | Output |
|---|---|--------|
| 0 | 0 | 1      |
| 0 | 1 | 0      |
| 1 | 0 | 0      |
| 1 | 1 | 0      |




XOR

| A | B | Output |
|---|---|--------|
| 0 | 0 | 0      |
| 0 | 1 | 1      |
| 1 | 0 | 1      |
| 1 | 1 | 0      |




XNOR

| A | B | Output |
|---|---|--------|
| 0 | 0 | 1      |
| 0 | 1 | 0      |
| 1 | 0 | 0      |
| 1 | 1 | 1      |

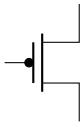

PMOS

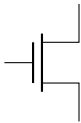

NMOS

| Parameter         | PMOS     | NMOS     |
|-------------------|----------|----------|
| Substrate Type    | n-type   | p-type   |
| Threshold Voltage | Negative | Positive |